

# Recitation 09

Combinational Logic

# Today's agenda

- ▶ We will discuss in recitation
  - ▶ Combinational Logic
    - ▶ Logic gates, truth tables, rules
- ▶ For homework Tonight
  - ▶ R10
    - ▶ Two parts
      - ▶ One - given an expression, produce the truth table
      - ▶ Two - given a truth table, write a logical expression for it

# Building Blocks

For combinational logic

# Combinational Logic

- ▶ There is no memory
  - ▶ That is, the outputs are a function ONLY of the **current** inputs, not of anything in the past
- ▶ Values are either true or false (but not both, or anything else)
  - ▶ We commonly represent true with 1 and false with 0
- ▶ There is at least one input and at least one output
  - ▶ But there can be more
  - ▶ Each input is either true or false
  - ▶ Each output should be defined for all possible values for the inputs!

# Combinational Logic

- ▶ There are three main ways to represent combinational circuits
  1. As a circuit diagram
  2. As a set of equations/expressions
  3. As a truth table


# Combinational Logic

- ▶ Logical expressions are build from a number of “gates”
- ▶ You are already familiar with the most important ones!
  - ▶ AND, OR, NOT
    - ▶ All boolean functions can be written with these three building blocks!
  - ▶ There are others, like XOR and NAND
    - ▶ All boolean functions can be written with just NAND!!!
- ▶ Letters/words are used to represent the inputs
  - ▶ For recitation homework, the variables are a single letter

# OR

- ▶ Output is 1 if ANY input is 1, 0 otherwise
- ▶ Output is 0 if ALL inputs are 0, 1 otherwise
- ▶ Output is the first 1 if there is one, last 0 otherwise (from the python world)
- ▶  $a$  or  $b$  is written as  $a + b$ 
  - ▶  $a | b$  or  $a \vee b$  are also common
  - ▶ Use  $a + b$  for recitation

a	b	a OR b
0	0	0
0	1	1
1	0	1
1	1	1

 

# AND

- ▶ Output is 0 if ANY input is 0, 1 otherwise
- ▶ Output is 1 if ALL inputs are 1, 0 otherwise
- ▶ Output is the first 0 if there is one, last 1 otherwise (from the python world)
- ▶  $a$  or  $b$  is written as  $ab$ 
  - ▶  $a \& b$  or  $a \wedge b$  are also common
  - ▶ Use  $ab$  for recitation

a	b	a AND b
0	0	0
0	1	0
1	0	0
1	1	1







# NOT

- ▶ Output is 1 if the input is 0, 0 otherwise
- ▶ A few ways to represent, both in text and graphically
  - ▶ Typically, as a “hat” on the input name, such as  $\bar{a}$
  - ▶ Can also be written with a prefix operator, such as
    - ▶  $\neg a$ ,  $!a$ , or  $\sim a$
  - ▶ For recitation homework, use  $\sim$
- ▶ Note that when drawing a not, it is common to see just the circle on the input or output of another gate

a	NOT a
0	1
1	0

 

# Circuit Diagram

 

- I stole this from the lecture, among the other pictures

## Expression

- ▶  $\sim ab + \sim b$
- ▶  $\bar{a}b + \bar{b}$

## Truth Table

a	b	$\sim ab + \sim b$
0	0	1
0	1	1
1	0	1
1	1	0

# Filling in a truth table

- ▶ First, list out all of the possible inputs
  - ▶ For  $N$  inputs, there are  $2^N$  possibilities
  - ▶ It helps to split things in two, that is, have space for the  $2^N$  possibilities, and for the first variable put 0 for the first half and 1 for the second half
    - ▶ For the next variable, put 0 for the first half of the previous variable's 0 group and 1 for the second half, then do the same for its 1 group
- ▶ Then, evaluate the expression for each possible inputs
  - ▶ This is tedious, so there are some shortcuts, especially if the expression is written nicely



# Filling in a truth table

- ▶ Groups of things ANDed together are typically called a clause
  - ▶ That is, clauses are things separated by ORs
- ▶ For each clause, see what the variables present are
  - ▶ For any variable that is negated, keep in mind that that variable is 0
  - ▶ For any other variable in the clause, keep in mind it is 1
  - ▶ Then, look through the truth table and wherever you see a row that has all of the variables in the clause with the right value, put a 1 for the output
- ▶ Then when you are out of clauses, fill in 0 for any output left



# Getting a circuit from a truth table

- ▶ For each output, look for where that output is 1 in the truth table
  - ▶ Look at the list of inputs - anywhere an input  $a$  is 1, write  $a$  in the clause
    - ▶ Anywhere an input  $a$  is 0, write  $\bar{a}$  in the clause
  - ▶ Say the output equals all of the clauses ORed together
  - ▶ Typically you can simplify, but that's a topic for a different day

