

Recitation 11

Sequential Logic

Today's agenda

- ▶ We will discuss in recitation
 - ▶ Sequential Logic
 - ▶ Finite State Machines
- ▶ For homework tonight
 - ▶ R11
 - ▶ You will create a truth table for a given finite state machine

Building Blocks

For sequential logic

Sequential Logic

- ▶ There is memory
 - ▶ Outputs depend on prior state as well as the current inputs
 - ▶ State can be stored and used later
- ▶ We rely on clock signals
 - ▶ Clock signals tell us when things should happen
 - ▶ We should only write to state when the clock is set a certain way

SR Latch

- ▶ Constructed from two NOR gates
- ▶ You can either **Set** the latch (make it remember 1), or **Reset** it (make it remember 0)
- ▶ Two inputs: S and R
- ▶ Two outputs: Q and NOT Q
 - ▶ Q is what it remembers, NOT Q is the opposite
- ▶ Both S and R cannot be 1 at the same time, or sadness occurs

D Latch

- ▶ Constructed from some additional logic and an SR Latch
- ▶ Two inputs: C and D
- ▶ You can have the latch remember D as long as C is true
- ▶ Two outputs: Q and NOT Q
 - ▶ Q is what the latch remembers, NOT Q is the inverse
- ▶ Ensures that S and R inputs to the SR Latch aren't both true

D Flip Flop

- ▶ Constructed from some additional logic and two D latches
- ▶ Same inputs and outputs as D latches
- ▶ But, the output is only stored on a chosen clock edge

Finite State Machines

Finite State Machines

- ▶ There are a number of states, inputs, and outputs
- ▶ To the beat of the clock, we read in inputs and go to new states, and set the outputs
- ▶ Both the output and the next state are defined by the current state and the inputs
- ▶ You can think of it as following a flow chart “when I’m on this step, and this is true, I go here”



An FSM Example

- ▶ The NYC Subway Turnstile
- ▶ There is a lock controlled by the FSM
- ▶ If the user didn't pay yet then the lock is active and the user can't push through
- ▶ If the user pays the lock unlocks until they push through
- ▶ Draw an FSM for this
- ▶ Write out a truth table
- ▶ Create the circuit

Another FSM Example

- ▶ Say we have an alarm system with a motion sensor
- ▶ The owner of the alarm system can press a button to arm the alarm
- ▶ The owner of the alarm system can press a different button to reset the alarm
- ▶ We want the alarm to go off if the motion sensor sees something, but only if the alarm has been armed
- ▶ If the owner resets the alarm, it both stops going off and is no longer armed
- ▶ The alarm goes off until the owner resets it
- ▶ Draw an FSM for this
- ▶ Write out a truth table
- ▶ Create the circuit